



ENGG*2450 Electric Circuits Concept Review

The Engineering Peer Helpers

Chapter 1 and 2 : Basic Concepts and Basic Laws

I. Concepts

- Resistors
 - Series and parallel
 - $1/R \rightarrow$ parallel
 - Using transformations to simplify complex circuits
 - Sources (dependent, independent)
 - Dependent is diamond \rightarrow rely on other circuit components (ex: $4i_1$)
 - Independent is circle
 - Current
 - Voltage and current division (helpful for later chapters in the course)
 - When you have to find a single voltage or current
 - With different branches and resistors etc.
 - Conductance
 - $1/R$ (reciprocal)
 - Convert if you are given in a question
 - Laws
 - Ohms ($V=IR$)
 - Kirchhoff's
 - Nodal (sum of the current at a node must sum to zero)
 - Loop (sum of voltage in a loop is equal to zero)
- 
- 

- Directions with voltages → stay consistent and work from defined directions

II. Tips and Tricks

- Textbook → summaries at end of chapters
 - Formulas, theories, laws, etc.
- Create summary sheets
- Practice with formula sheet
- State assumptions and define any conventions you are using
- Identify each formula, identify each of the units & know what every variable represents


III. Blank Space – Formulas, Diagrams etc.

- Transformation formulas
- Conventions (CW and CCW)

Chapter 3 : Methods of Analysis

IV. Concepts


- Nodal Analysis
- Supernode
 - Source in between components in cct and not attached to ground
 - From chapters 1 and 2 can use laws and theorems to solve
 - Use KCL and KVL and then that source gives you nodal voltage and then nodal analysis without a supernode
- Mesh Analysis
 - When to use nodal versus mesh analysis?
 - A cct w fewer nodes than meshes is usually better with nodal analysis
 - Mesh is an independent loop within the cct → more cubic of a cct

- 
- Usually have to use linear algebra to solve system of equations from mesh analysis
 - Supermesh
 - When you have two meshes that share a current source → when you create a supermesh
 - Has no current of its own
 - Exclude source and any elements in series with it

V. Tips and Tricks

- Highlight ground branch and then anything connected to that you know is not a supernode bc connected to ground
- Colour code circuits to better visualize
- Node voltages asked? Maybe use nodal analysis
- Mesh/branch current asked? Mesh analysis may be better
- Interchanging methods or using both to get final answer
- Stay consistent with your class notes
- High to low potentials
- Identify nodes and branches in the loops and depending on the cct will decide whether or not nodal or mesh analysis may be better
- Take time before you approach a problem to make a plan for how to solve
- Collaborate and study with people in your course
- Nodal analysis you cannot do transistor applications (in further chapters)


VI. Blank Space – Formulas, Diagrams etc.

- Consistent with voltages
 - Defining assumptions and conventions
- 


Chapter 4 : Circuit Theorems

VII. Concepts

- Thevenin/Norton
 - $R_{th}=R_n$
 - Relate load of cct to voltage source and resistor
 - Norton finds current and Thevenin finds voltage
 - Working with parallel versus series
 - One of the best ways to simplify a cct
 - The terminals → make sure you do Thevenin and Norton between the terminals and not the entire cct
- Superposition
 - Summation of simpler circuits
 - When you have lots of sources within a cct (current or voltage sources)
 - “Turn off” independent sources except one
 - Only consider one independent source at a time and then replace those voltage sources → either a short circuit (V) or open circuit (I)
 - Leave dependent sources in
 - Will change if you were to take them out
 - Use KVL and KCL depending on question
 - Time consuming method
- Source transformations
 - Important for future courses
 - Relies on equivalence
 - Using Thevenin and Norton to transform voltage sources into current sources
 - $V_s=ir$
 - $I_s=v/r$

- 
- Voltage source and resistor in series can be transformed to current source and resistor in parallel
 - Can be related to delta y simplifications
 - When converting does not increase the simplicity → use another method
 - Linearity
 - Relation between output and input (directly)
 - Direct proportionality (ohms law is linear $V=IR$)
 - Quadratic relationships you cannot use this strategy
 - Important for theory-based questions when relating different values and elements within the cct
 - Scalar multiples etc. for conceptual questions
 - Homogenous formulas

VIII. Tips and Tricks

- Relationship based questions → hint for linearity-based questions
 - Note if they ask you to use certain methods within the question
 - With source transformations you can change how cct looks to something you are more comfortable with
 - Comfortable switching between Thevenin and Norton
 - Figure out what the question is asking you specifically
 - Textbook is very helpful for this chapter
 - Source transformations rely on equivalent resistances and current/voltage division
 - Concepts used for larger ccts
 - If it becomes more complicated → may be better to use a different method
- 



IX. Questions and Contact

- a) This will be posted on The Engineering Peer Helpers (EPH) Website.
 - i) <https://www.uoguelph.ca/engineering/content/current/peer-helper>
 - b) There will not be a filled in version posted. Please write notes during the session.
 - c) Stay tuned for more ENGG*2450 workshops/sessions before the final exam.
 - d) Email for a small-group consultation. It's great to think of your questions and send them beforehand!
 - e) Book a one-on-one consultation for circuits!
- 